



# Presentation of Bachelor Project Work

UNIVERSITÄT  
DUISBURG  
ESSEN

Prepared by  
**Godwin Maxime Arinaitwe**  
with  
**Prof. Dr.-Ing. K. Solbach**  
department of  
High-Frequency Engineering  
at the  
University of Duisburg-Essen

Topic:

**Development of a  
Transmit/Receive Switch for  $^{23}\text{Na}$   
Coils in a 7-Tesla Magnetic  
Resonance Imaging System (MRI)**

# Outline


- **Introduction**
  - ✓ Motivation
  - ✓ Methodology
- **Concept**
  - ✓ MRI
  - ✓ PIN Diodes
  - ✓ S-Parameters
- **Hardware Development**
  - ✓ Schematic design & simulation
  - ✓ Board layout & optimisation
  - ✓ Wire-wound Inductors
- **Measurements & results**
  - ✓ S-Parameter tests
  - ✓ High Power Test
- **Conclusion**
- **Questions**



# Motivation
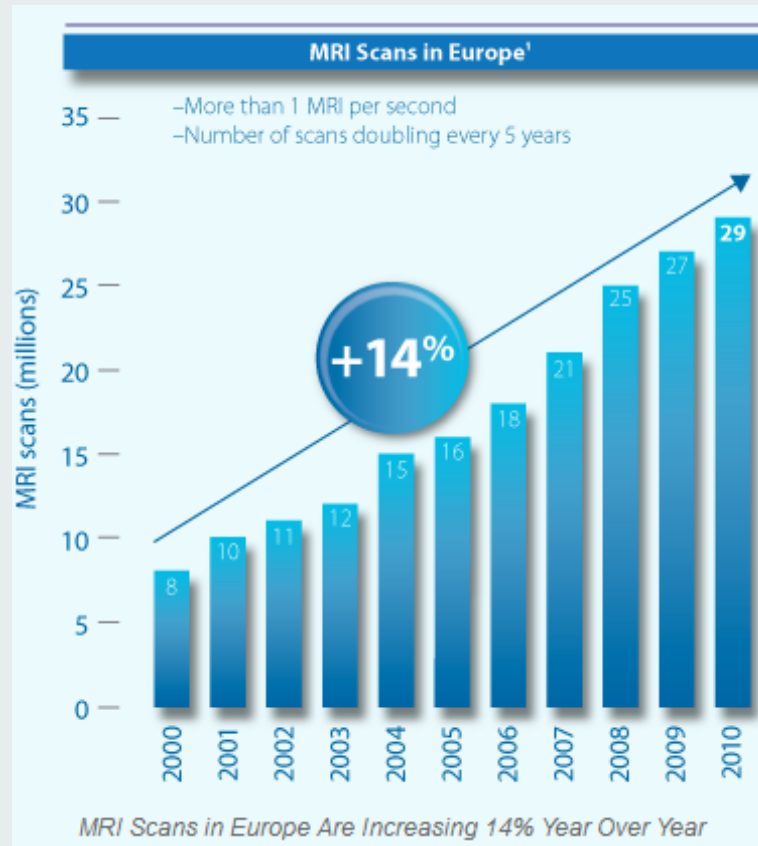
## MRI – Magnetic Resonance Imaging

- ❖ Sets the **standard** of care for diagnostic imaging
- ❖ One of the **fastest growing** areas in diagnostic imaging
- ❖ Needs a **fast switch** between transmission and receive for proper functionality



Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions



- **RF Simulation of circuit in ADS**
- **Band-pass Filter Optimisation**
- **Realisation of optimised circuit on micro-strip**
- **PCB layout design in EAGLE**
- **Assembly of Circuit**
- **Testing for Impedance/Reflection Coefficients and Insertion Loss**
- **Circuit pass-band frequency tuning**
- **High Power Test**

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions



# MRI - Magnetic Resonance Imaging

- **Imaging technique** used primarily in medical settings
- Produces **high quality images** of the inside of the human body
- Available in different types including **1.5-Tesla, 3-Tesla** and **7-Tesla**
- **Major manufacturers** include Siemens, GE Healthcare, Phillips, Toshiba and Hitachi



7-Tesla MRI from Siemens

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions




# MRI - Magnetic Resonance Imaging


## Comparison to CT-Scan

- MRI – **magnetic energy and RF** vs. CT-Scan – Ionisation radiation that means added risk as x-ray dose is cumulative
- MRI – **superior for soft tissue evaluation** vs. CT-Scan – better for bony tissue

MRI Scan Image

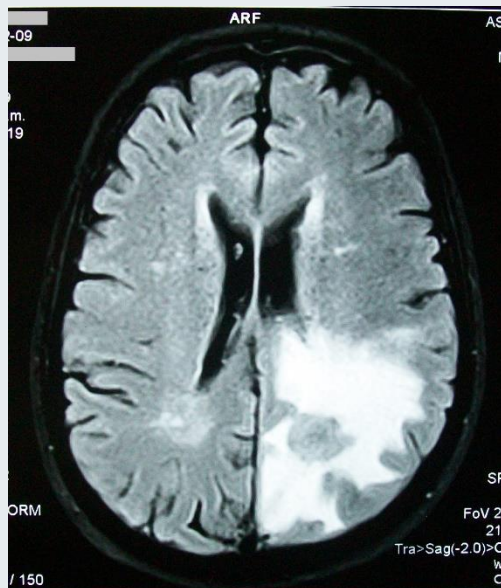

CT-Scan Image

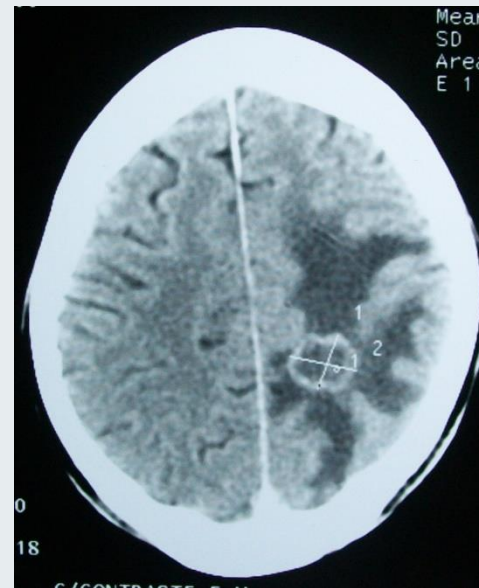

VS.

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions




# MRI - Magnetic Resonance Imaging

## Basic Functionality of MRI

### Summarised in 5 Steps:

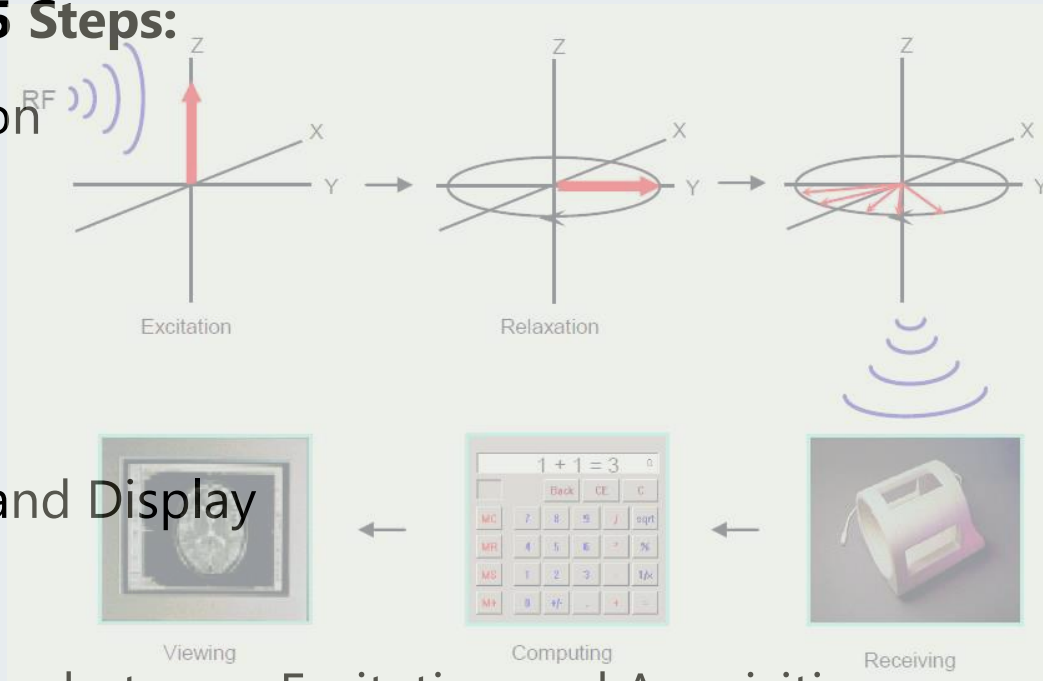- i. Magnetisation
- ii. Excitation
- iii. Relaxation
- iv. Acquisition
- v. Computing and Display



Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions

**Small time frames** between Excitation and Acquisition


necessitates a **QUICK switch** between **Transmission of RF Pulse** and **Receive of Released RF energy from H-atoms**




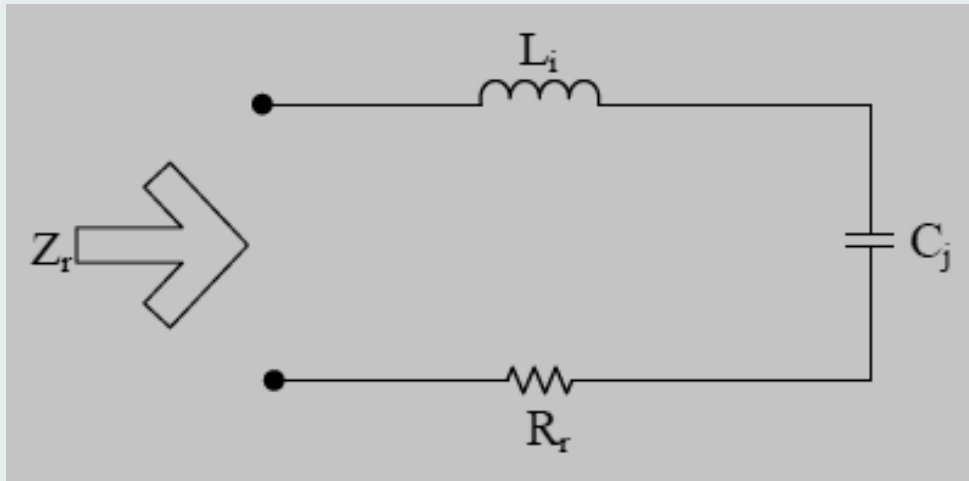
# PIN Diodes

- **Wide & lightly doped intrinsic** region between p- and n-type semiconductor regions
- Applications include **RF switches**, power limiters, modulators and variable attenuators
- In **Reverse bias**, a **series capacitance** leads to high **diode impedance**



Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion


Questions



- Reverse bias = **OFF state** in an RF Switch
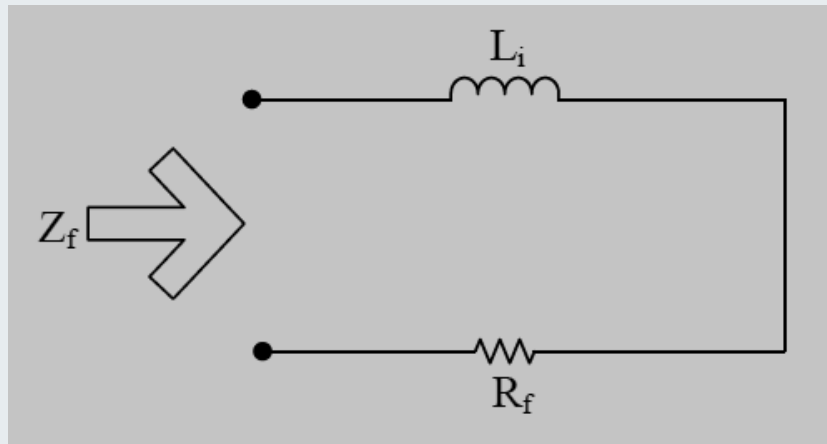
# PIN Diodes

- In **Forward bias**, current removes the junction capacitance and leaves the diode in a **low impedance state**



- Forward bias = **ON state** in an RF Switch

## Advantages of PIN Diodes:

- High operational speeds (range from **1 $\mu$ s to 10 $\mu$ s**)
- Small size  $\equiv$  can easily be embedded in RF circuits
- control large RF signals with small DC excitation levels

Introduction

Concept

Hardware  
Development

Measurements  
& Results


Conclusion

Questions


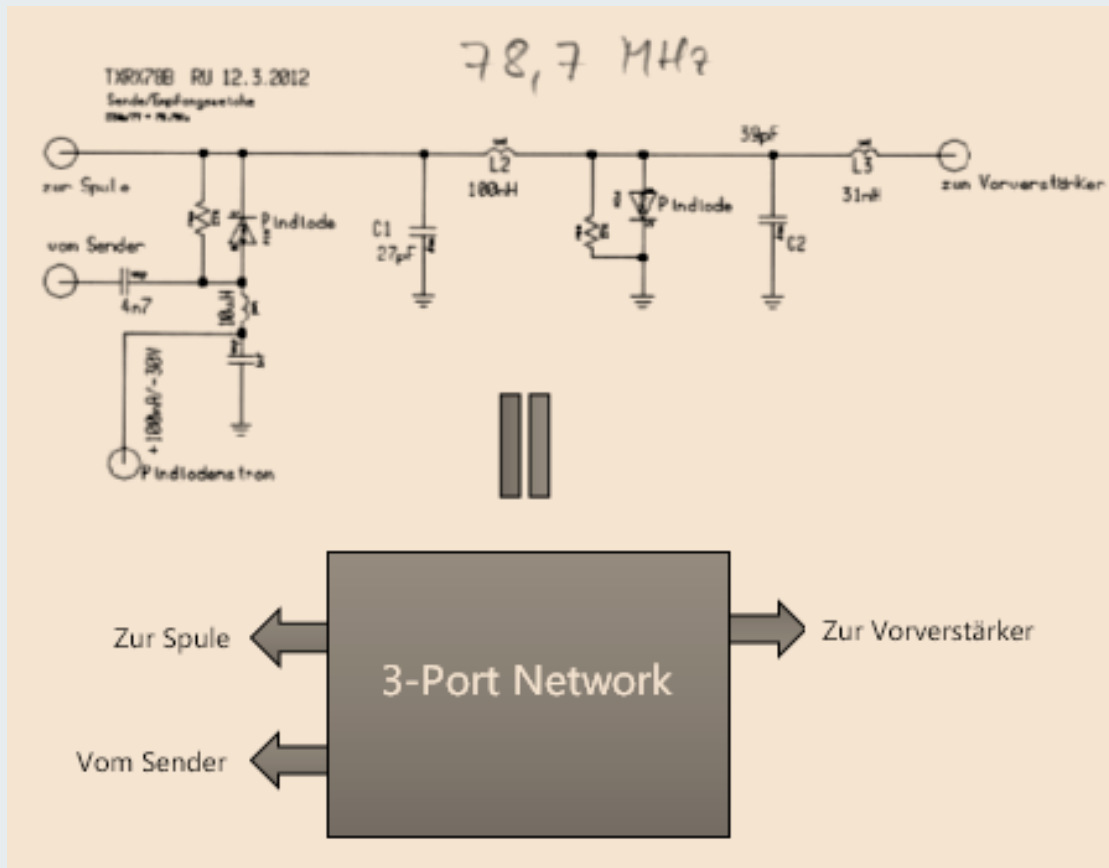
# S-Parameters

- Provide complete description of an N-network as seen from its N-Ports



Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions



# S-Parameters

- Represented in an S-Matrix

$$(S_{11}) \quad (\text{One-port})$$

$$\begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \quad (\text{Two-port})$$

$$\begin{pmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{pmatrix} \quad (\text{Three-port})$$

- $S(1,1)$ ,  $S(2,2)$ ,  $S(3,3)$  represent the **Reflection Coefficients** of the network
- $S(1,2)$ ,  $S(2,3)$ ,  $S(1,3)$  represent the **Transmission Coefficients** of the network
- **Insertion Loss** can be calculated using:

$$\text{Insertion Loss (IL)} = -20 \log_{10} |S(1,2)| \text{ dB}$$

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions



# Hardware Development

Involved the following:

- ❖ **Schematic Design in ADS 2009**
- ❖ **S-Parameter simulations in ADS 2009**
- ❖ **Board Layout in EAGLE**
- ❖ **Layout Optimisation**
- ❖ **Making Wire-wound Inductors**

Advanced  
Design  
System  
2009

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion


Questions



EAGLE
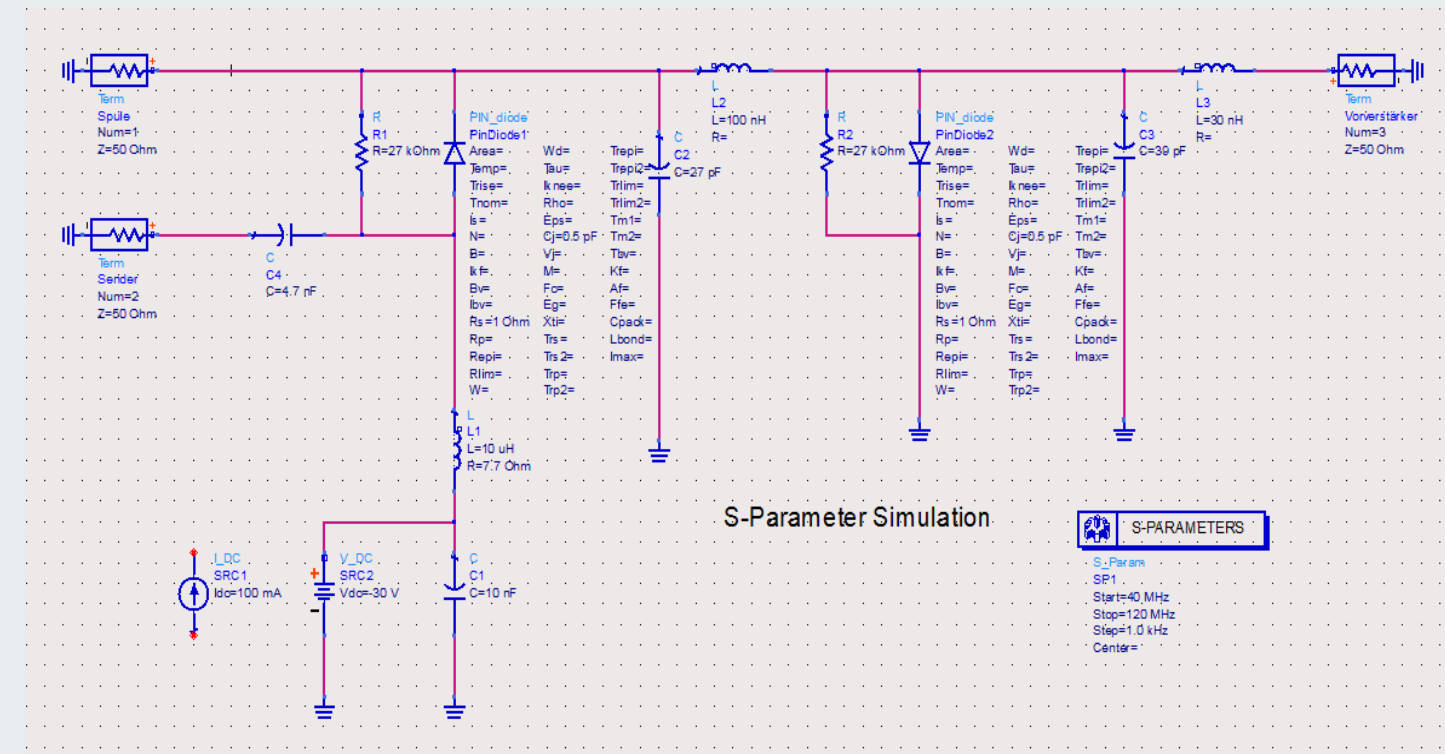
# Schematic Design & Simulation

- Carried out using **Advanced Design System**
- Schematic of provided circuit is drawn



- **S-Parameter Simulations** are then carried out using Simulation tool of ADS 2009

Introduction

Concept

Hardware  
Development

Measurements  
& Results


Conclusion

Questions




# ADS 2009 S-Parameter Simulation Results – Forward Biased


$S(1,1) = -15.6\text{dB}$

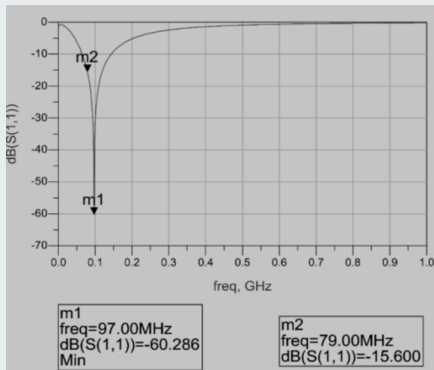


$S(1,2) = -0.39\text{dB}$

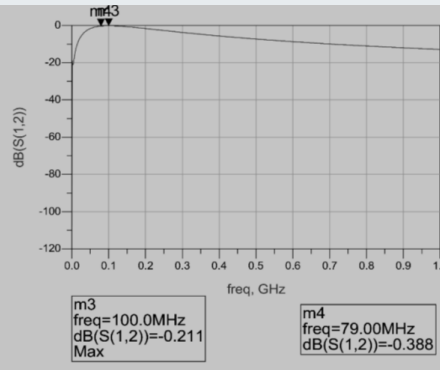


$S(2,2) = -16.1\text{dB}$

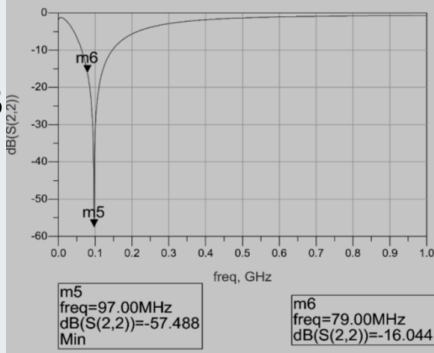


$S(2,3) = -29.7\text{dB}$

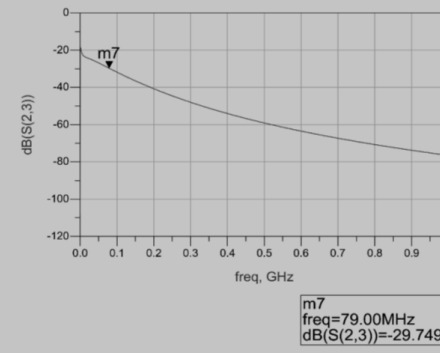

$S(1,3) = -29.6\text{dB}$

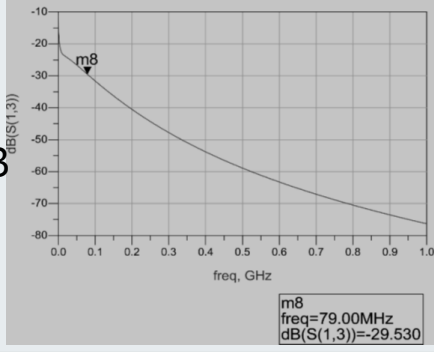

$S(3,3) = -0.57\text{dB}$

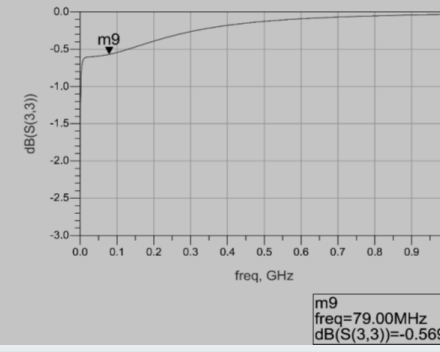


- Introduction
- Concept
- Hardware Development
- Measurements & Results
- Conclusion
- Questions




# ADS 2009 S-Parameter Simulation Results – Reverse Biased


$S(1,1) = -45.5\text{dB}$

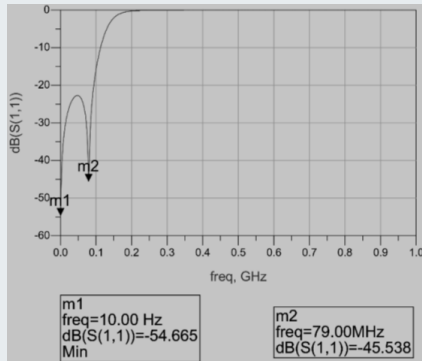


$S(1,2) = -38.0\text{dB}$

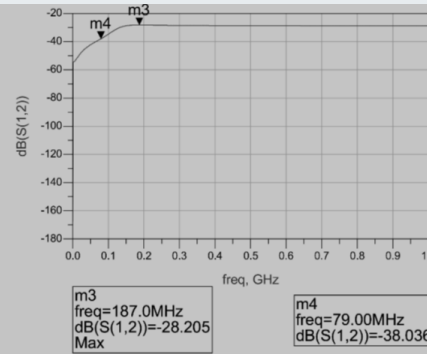


$S(2,2) = -0.03\text{dB}$

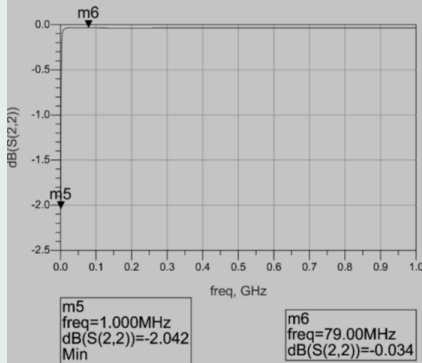


$S(2,3) = -38.0\text{dB}$

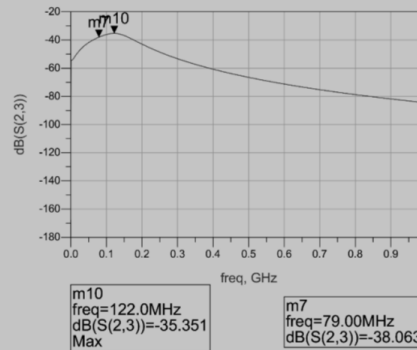

$S(1,3) = -0.02\text{dB}$

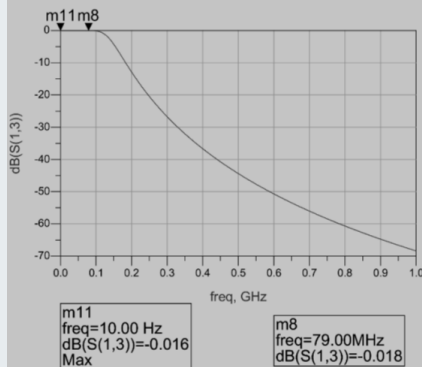

$S(3,3) = -43.7\text{dB}$

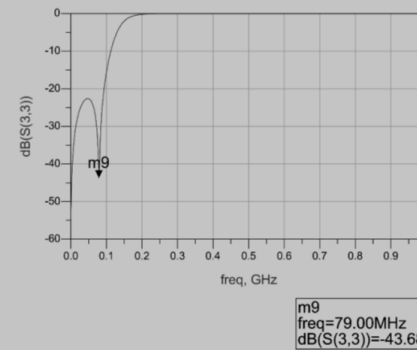

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion


Questions





## Optimised Circuit layout board drawn using EAGLE

First Version:

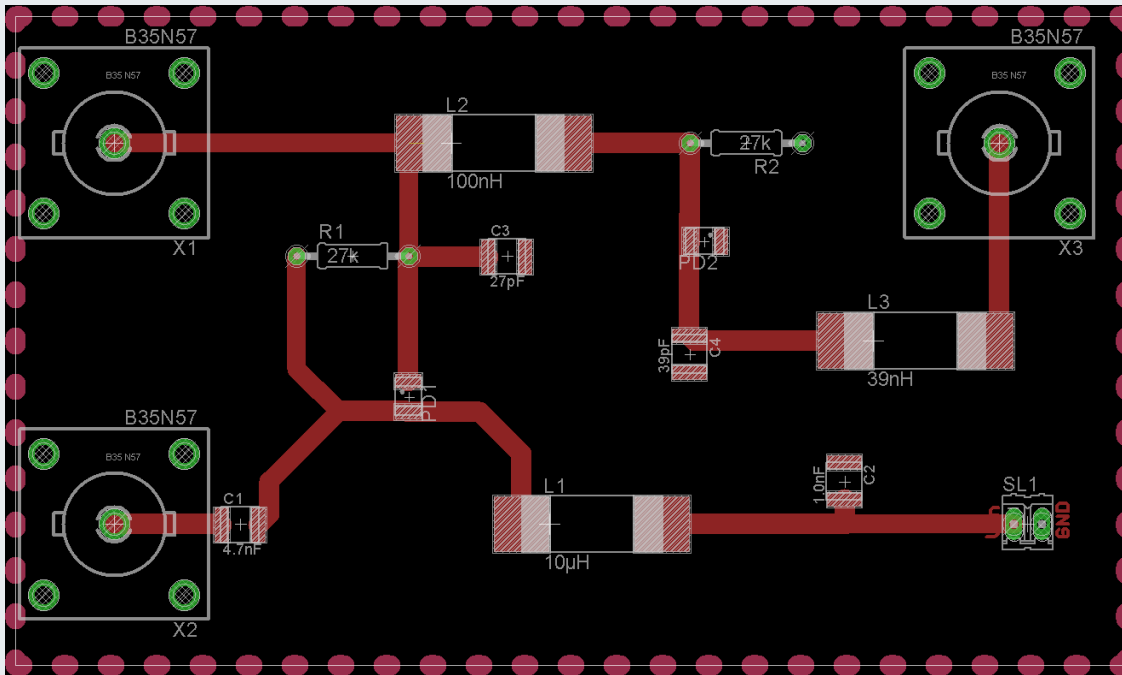

- Circuit components way far apart
- Micro-strip width far too small to support  $50\Omega$  impedance matching

Introduction

Concept

Hardware  
Development

Measurements  
& Results


Conclusion

Questions



# Board Layout & Optimisation

## X-Version (Improved & Final Version)

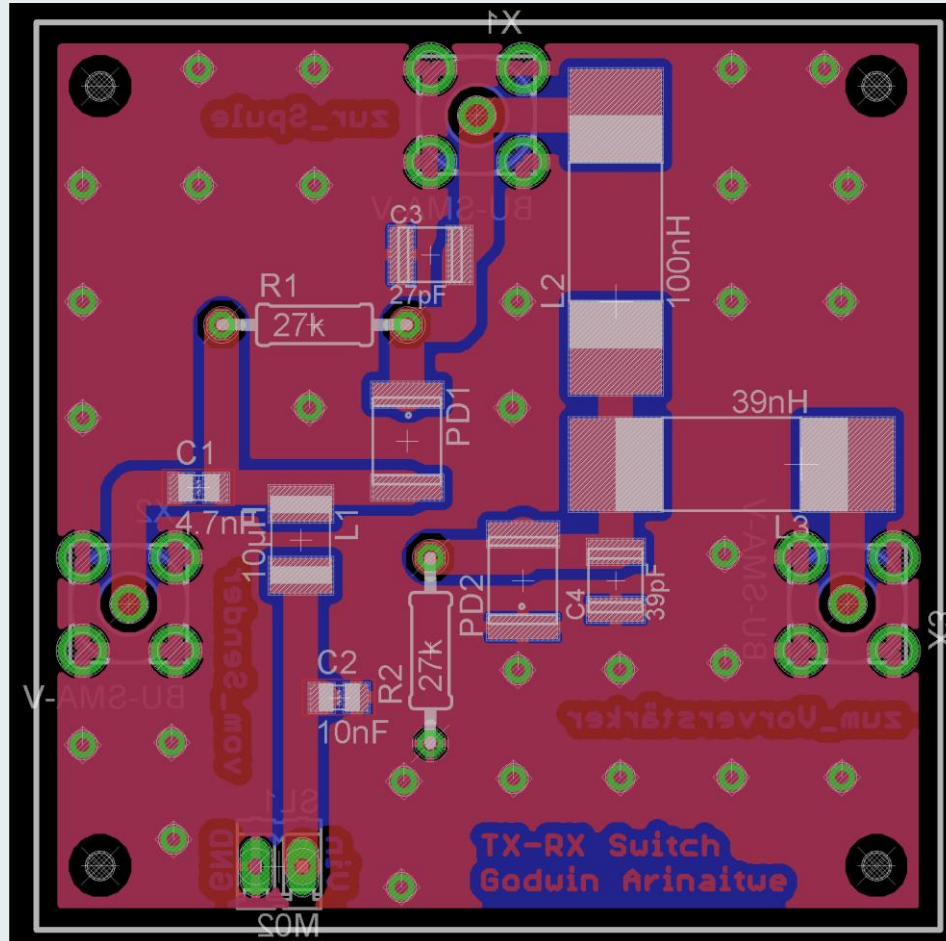

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions



# Wire-wound Inductors

- required number of turns calculated using formula below:

$$N = \frac{1}{a} \cdot \left( \sqrt{\frac{L \cdot (22.9 \cdot a + 25.4 \cdot l)}{10^{-6}}} \right)$$

where;


$N$  = number of turns

$l$  = length in cm

$a$  = radius of coil in cm

- derived from formula to calculate inductance of a circular coil with a single layer turn
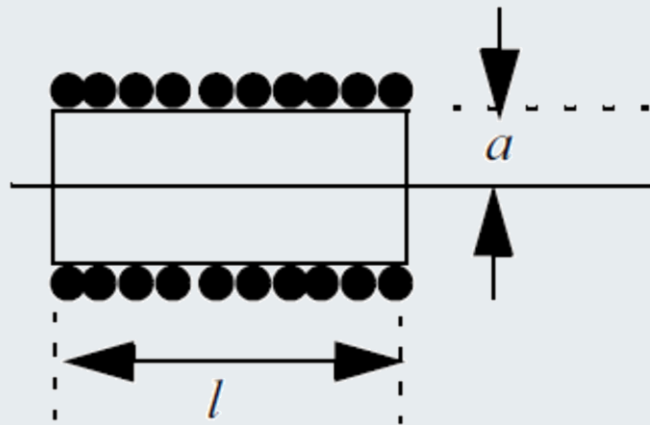
$$L = \frac{(a \cdot N)^2}{(22.9 \cdot a + 25.4 \cdot l)} \mu H$$



Introduction

Concept

Hardware  
Development

Measurements  
& Results


Conclusion

Questions



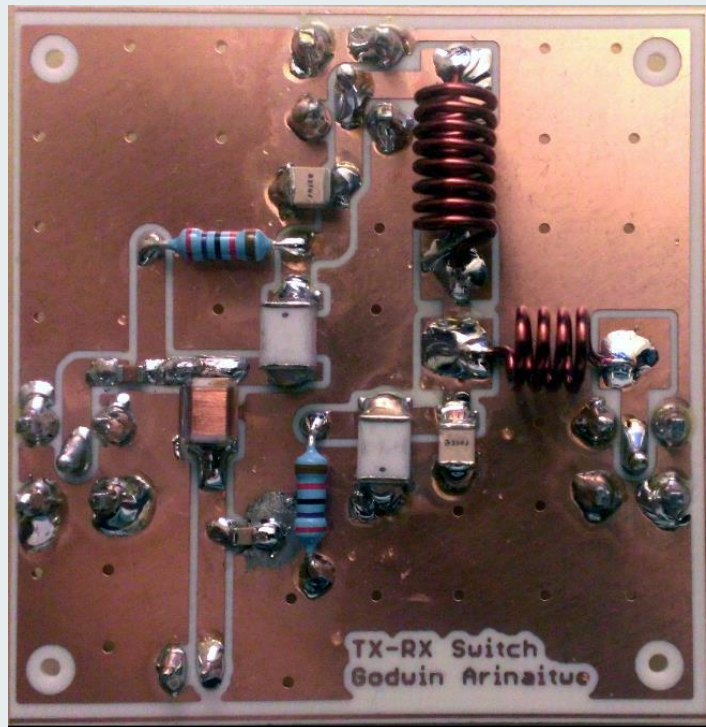
# Wire-wound Inductors – Final Product

- Inductors (Coils) are wire-wound and finally...
- Circuit components are soldered onto board



Top Layer

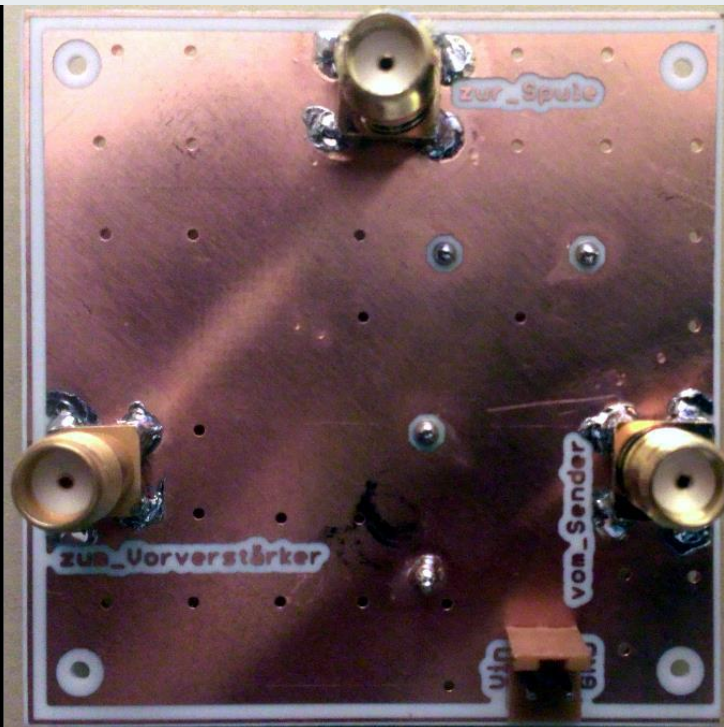

Bottom Layer

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions





# Measurements & Results

Tests carried out on the Tx/Rx switching circuit:

- **S-Parameter Tests**
- **Circuit bandpass frequency Tuning**
- **High Power Test**

Introduction

Concept

Hardware  
Development

Measurements  
& Results


Conclusion

Questions


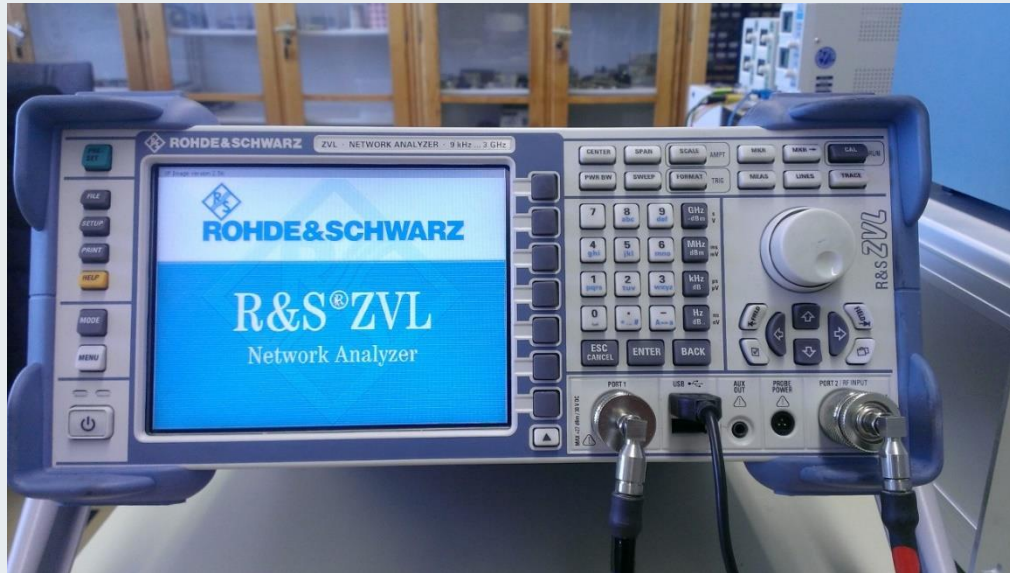
# S-Parameter Tests - Setup

- Small-signal Vector network Analyser used to carry out measurements



- Carried out for both Forward Biased state and Reverse Biased State
- 3-Port circuit necessitated additional measurement states like Port-1 Terminated, Port-2 Terminated and Port-3 Terminated states

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion


Questions



# S-Parameter Tests - Setup

- ON state -> Circuit is biased (voltage/current applied)
- OFF state -> Circuit is not biased (floating)

## Measurement Setup:

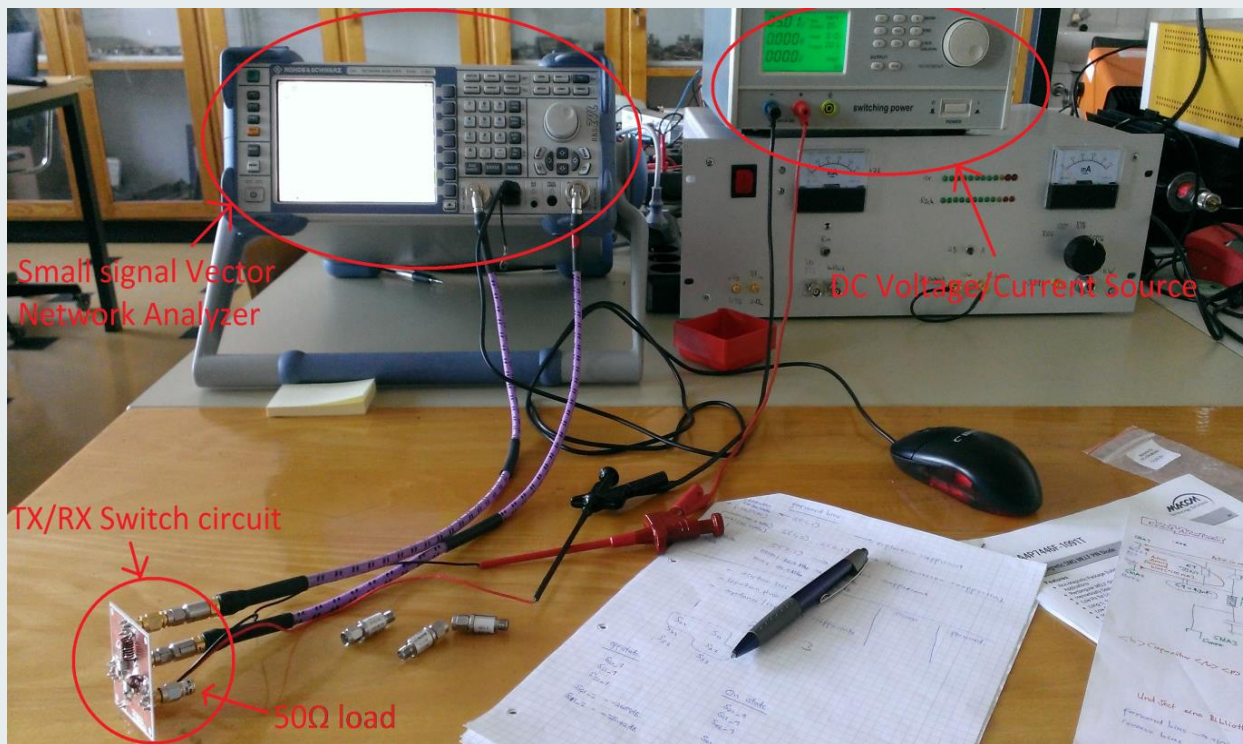

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions



# S-Parameter Tests - Results

Forward biased circuit

Terminated Port	S-Parameter	Magnitude (dB)	
		ON State	OFF State
<b>Port_1</b> <i>(Zur Spule)</i>	$S_{22}$	-0.211	-16.296
	$S_{23}$	-34.966	-28.078
	$S_{33}$	-31.321	-0.267
<b>Port_2</b> <i>(vom Sender)</i>	$S_{11}$	-28.370	-15.376
	$S_{13}$	-35.048	-0.279
	$S_{33}$	-0.180	-14.083
<b>Port_3</b> <i>(zum Vorverstärker)</i>	$S_{11}$	-26.188	-16.296
	$S_{12}$	-0.175	-26.464
	$S_{33}$	-23.973	-0.256

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions





# S-Parameter Tests - Results

Reverse biased circuit

Terminated Port	S-Parameter	Magnitude	
		ON State	OFF State
Port_1 <i>(Zur Spule)</i>	S <sub>22</sub>	-16.258	-0.284
	S <sub>23</sub>	-27.978	-27.779
	S <sub>33</sub>	-16.252	-16.218
Port_2 <i>(vom Sender)</i>	S <sub>11</sub>	-15.549	-15.582
	S <sub>13</sub>	-0.247	-0.270
	S <sub>33</sub>	-14.734	-14.741
Port_3 <i>(zum Vorverstärker)</i>	S <sub>11</sub>	-16.509	-16.587
	S <sub>12</sub>	-26.631	-26.413
	S <sub>33</sub>	-0.242	-0.289

Introduction

Concept

Hardware  
Development

Measurements  
& Results


Conclusion

Questions


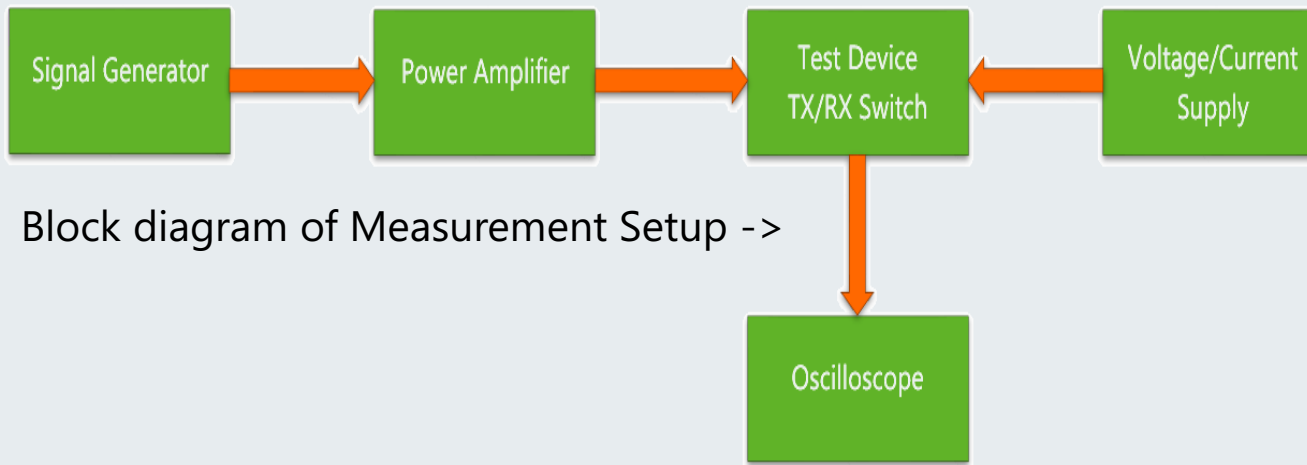
# High Power Test – Setup

- Verifies the power handling capabilities of the switch



- Signal at **78.7 MHz** is generated from an **Agilent N9310A Signal Generator** and is then fed to an amplifier
- Output from the **ZHL-100W-52 amplifier from Mini Circuits Inc.** which can deliver close to 100W RF power CW when driven at 0 dBm input is fed to the switch.
- Switch is biased by applying either **-30V for reverse bias** or **100mA for Forward bias**

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusion

Questions



# High Power Test – Setup

## Final measurement setup for High Power Test



The **amplitude of signal generator** is gradually **increased** from **-20 dBm** and observations are made

Introduction

Concept

Hardware  
Development


Measurements  
& Results

Conclusion

Questions



# High Power Test – Results

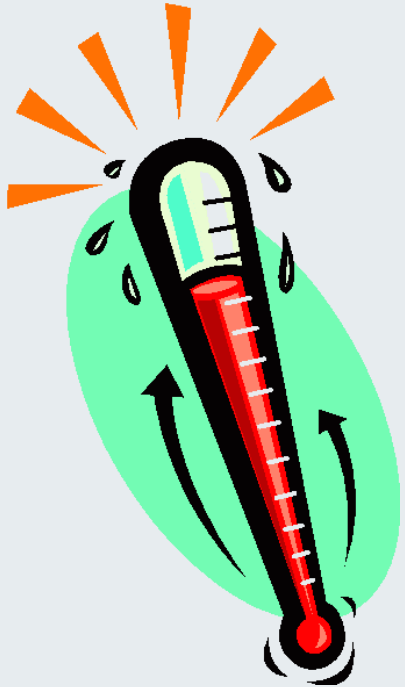

- **Heating** noticed at the PIN diodes
- Signal at oscilloscope gradually fades as the amplitude of signal generator passes **-5dBm** mark or **30W Continuous Wave** output at Amplifier

Introduction

Concept

Hardware  
Development

Measurements  
& Results


Conclusion

Questions


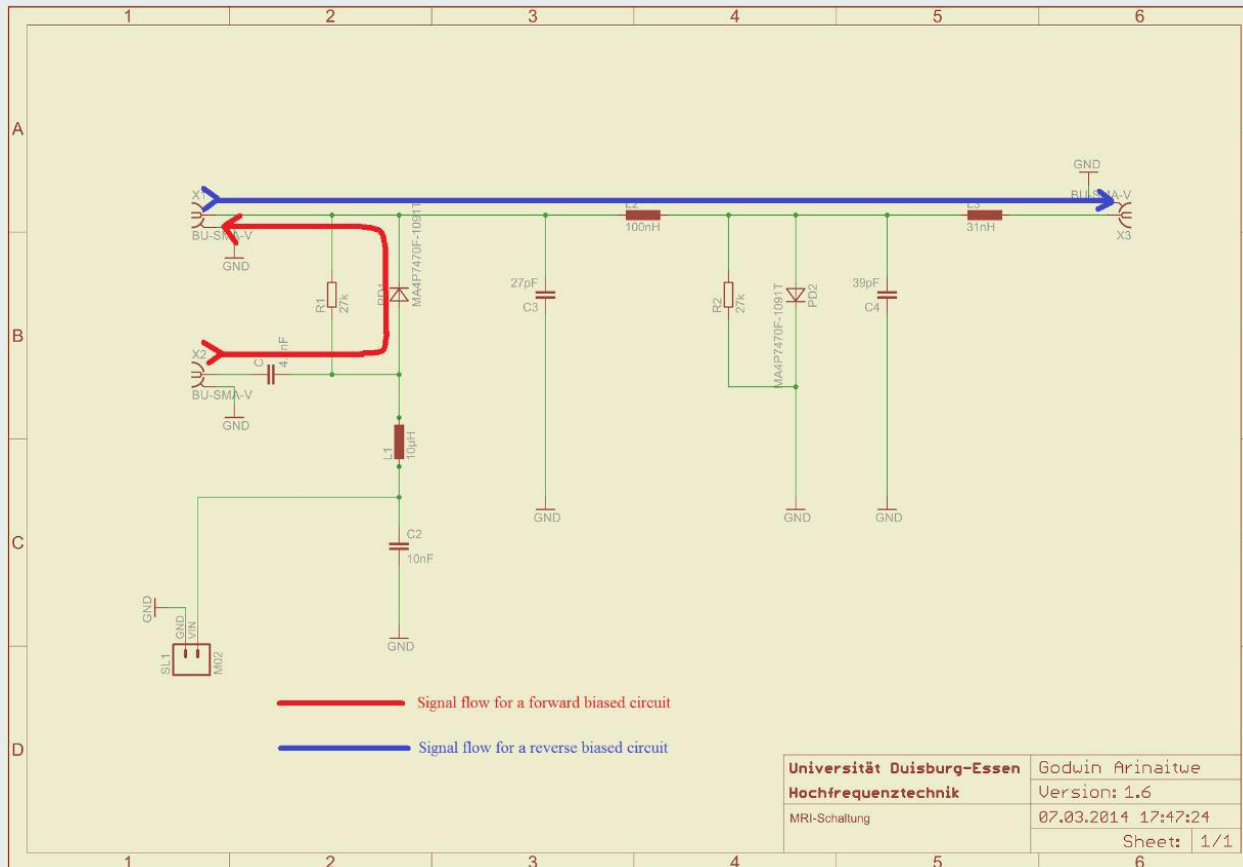
# Conclusions – S-Parameters Interpretation

- ❖ **S-Parameter Simulations** in ADS and **S-Parameter Measurements** on the Vector Network Analyser show **Circuit Functionality** as illustrated below.



Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusions

Questions



# Conclusions

- ✓ Circuit is **feasible** as a fast switch between Transmission and Receive in an MRI **up to about 30W** output at the amplifier
- ✓ This refers to a **Continuous Wave signal** while in reality **Pulsed Wave signals** are sent in an MRI
- ✓ Implies: **Average power** of the MRI  $< 30\text{W}$ . Such a case could be a **duty cycle of just 3%** and a **peak power of 1kW**

Introduction

Concept


Hardware  
Development

Measurements  
& Results

Conclusions

Questions



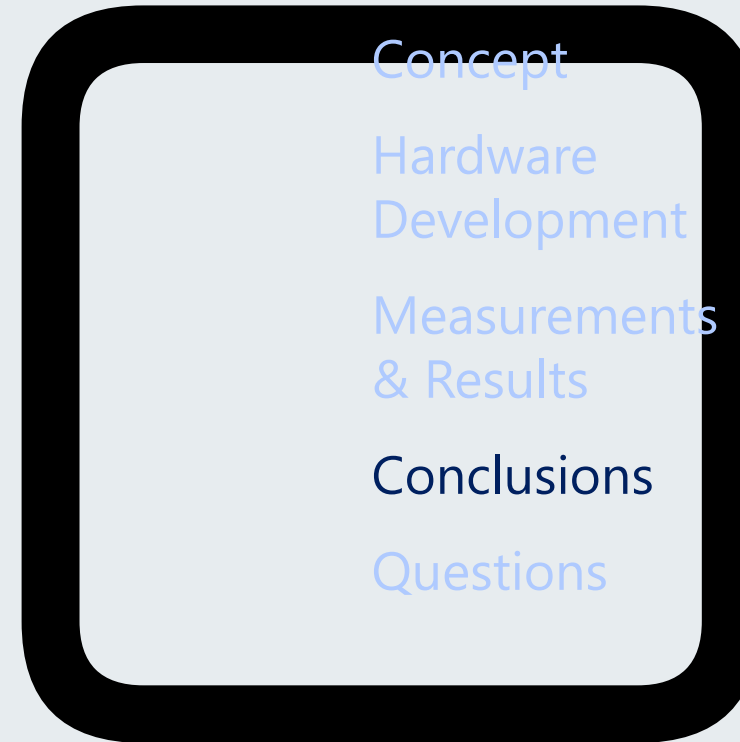

Introduction

Concept

Hardware  
Development

Measurements  
& Results

Conclusions

Questions

